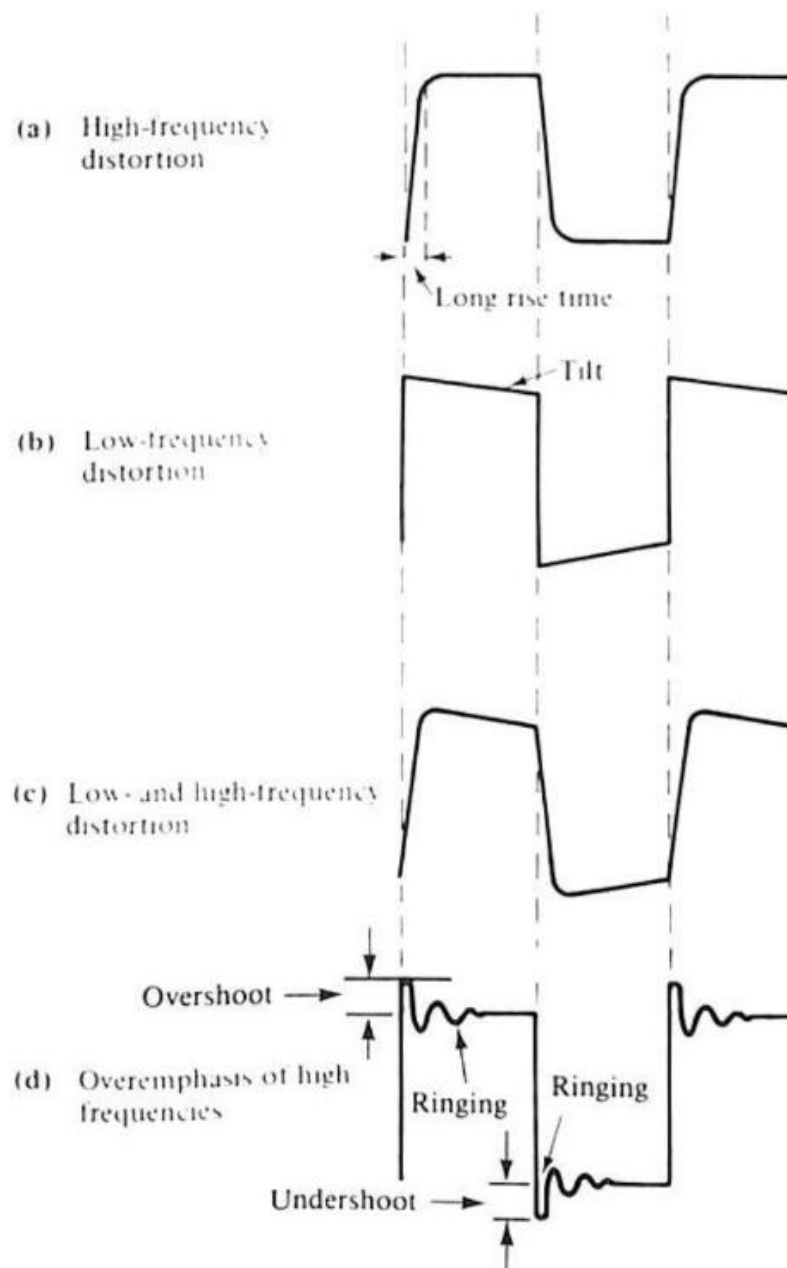


What happens when a square wave is applied to circuitry that does not pass all the necessary frequency components? The resultant output is a distorted square wave.

- Three main types of waveform distortions:

Sec. 1-4 Waveform Distortion



- **Increased Rise & Fall Times** t_r & t_f as seen in image a, is due to High Frequency Distortion.
 - **High Frequency Distortion** is caused by parallel capacitance.
- **Tilt** indicates Low Frequency Distortion.
 - **Low Frequency Distortion** is caused by series capacitance.
- **Ringing** is High Frequency Distortion and occurs when a circuit oscillates for a short time due to the presence of stray inductance and capacitance.
- When circuits overemphasize some of the high-frequency harmonics, **Overshoots** and **Undershoots** are produced.

References:

Bell, D. A. (1997). *Solid state pulse circuits*. Sarnia, ON: David A. Bell.