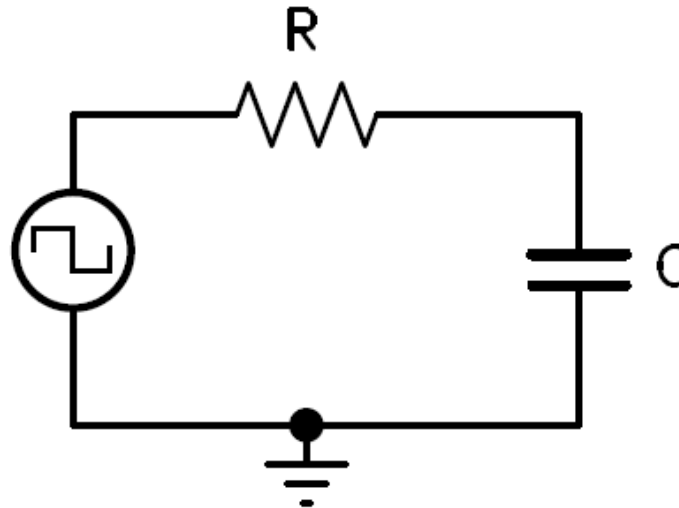


Consider the following circuit:



Integration (think averaging!)

- “Integration is the summation of area.” (Bell p.50)
- There is not enough time for the capacitor to fully charge or discharge.
 1. PW or PS is less than 5τ .
 2. “An integrating circuit is an RC circuit with the output taken across the capacitor and $RC \geq (10 \times PW)$ ”(Bell p.53)
 3. The standard formulas for designing an Integrating RC circuit is:
 - $RC = \tau$
 - 50% DC, $PW = PS$
 - $PW = \text{Time to charge}, PS = \text{Time to discharge}$
 - $RC \geq (10 \times PW)$ (Integration in terms of τ)
 - $\text{Time} = \frac{1}{10} \tau$ (Integration formula in terms of Time, not enough Time to charge or discharge)
 4. Additional formulas (derived previously):
 - $\# \text{ of cycles?} = \frac{5\tau}{\text{Period}} (\text{cycles})(\text{stabilization})$
 - $V_{max} = \frac{V_{gen+} - t}{1 + e^{\frac{-t}{RC}}}$
 - $V_{min} = V_{gen+} - V_{max}$

See Image:

- a) Is **not** an Integrator, the capacitor is fully charging and discharging.
- b) Is **not** an Integrator, $\tau = \text{PW}$. 63% charge and discharge
- c) Is an **Integrator**, V_{max} and V_{min} will alternate minimally equal distance above and below the average input generator voltage.

Sec. 2-5 Integrating Circuits

