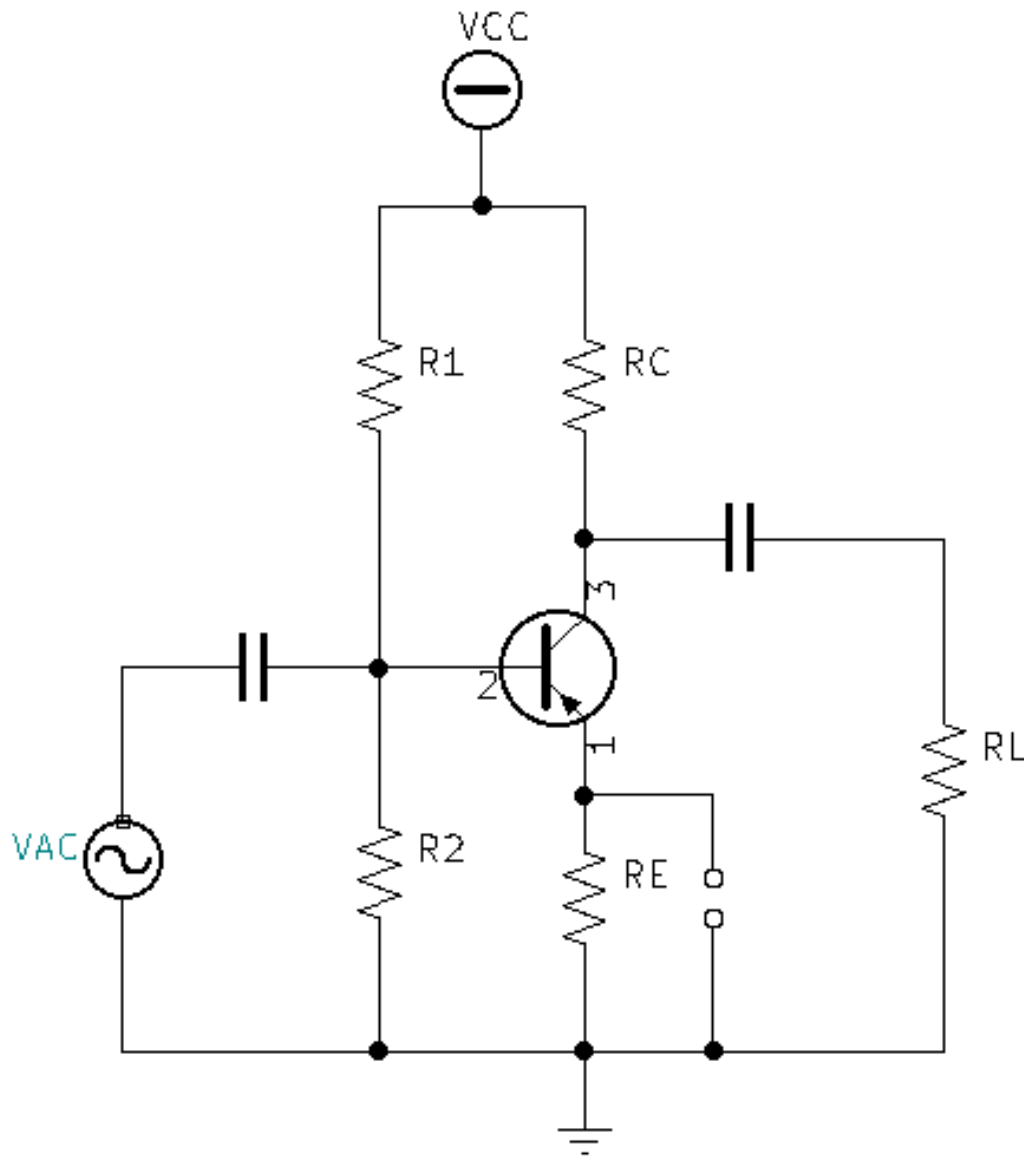


Emitter Peaking:



- Calculate and or Measure your existing f_{ch} .
- Determine your predicted *new* f_{ch} will be if emitter peaking is added:
 - If $-3dB$ is elevated to $0dB$, then the existing $-6dB$ will become the new $-3dB$
 - Find the $-6dB$ frequency f at the existing f_{ch}

- $-6dB = 20\log \frac{1}{\sqrt{1+(\frac{f}{f_{ch}})^2}}$
- $\frac{-6}{20} = \log \frac{1}{\sqrt{1+(\frac{f}{f_{ch}})^2}}$
- $\frac{-6}{20} = \log \frac{1}{\sqrt{1+(\frac{f}{f_{ch}})^2}}$
- $1 \times 10^{\frac{-6}{20}} = \frac{1}{\sqrt{1+(\frac{f}{f_{ch}})^2}}$
- $\sqrt{1+(\frac{f}{f_{ch}})^2} = \frac{1}{1 \times 10^{\frac{-6}{20}}}$
- $1+(\frac{f}{f_{ch}})^2 = (\frac{1}{1 \times 10^{\frac{-6}{20}}})^2$
- $(\frac{f}{f_{ch}})^2 = \left(\frac{1}{1 \times 10^{\frac{-6}{20}}}\right)^2 - 1$
- $\frac{f}{f_{ch}} = \sqrt{\left(\frac{1}{1 \times 10^{\frac{-6}{20}}}\right)^2 - 1}$
- $new\ fch_{emitter\ peaking} = fch \sqrt{\left(\frac{1}{1 \times 10^{\frac{-6}{20}}}\right)^2 - 1}$
- $Improvement\ Factor\ (k) = \frac{new\ fch_{emitter\ peaking}}{fch} = \frac{fch \sqrt{\left(\frac{1}{1 \times 10^{\frac{-6}{20}}}\right)^2 - 1}}{fch}$
- $Improvement\ Factor\ (k) = \frac{fch}{fch} \times \frac{\sqrt{\left(\frac{1}{1 \times 10^{\frac{-6}{20}}}\right)^2 - 1}}{1}$
- $Improvement\ Factor\ (k) = \frac{\sqrt{\left(\frac{1}{1 \times 10^{\frac{-6}{20}}}\right)^2 - 1}}{1}$
- $Improvement\ Factor\ (k) = \sqrt{\left(\frac{1}{1 \times 10^{\frac{-6}{20}}}\right)^2 - 1}$
- **$Improvement\ Factor\ (k) = 1.72658$**

- Determine the Emitter Peaking Capacitor value:
 - In-order to achieve a 3dB boost and an
Improvement Factor (k) = 1.72658 using Emitter
 Peaking we need find an Emitter Peaking Capacitor
 that will be resonant with R_E at the original or old f_{ch} .
 - Find Emitter Peaking Capacitor:
 - $X_{C_{EP}} = R_E$, at resonance f_r
 - $X_{C_{EP}} = \frac{1}{2\pi f_c}$
 - $R_E = \frac{1}{2\pi f_r C_{EP}}$
 - $C_{EP} = \frac{1}{2\pi f_r R_E}$
 - $C_{EP} = \frac{1}{2\pi(\text{old } f_{ch})R_E}$