

FIND:

IR1:\_\_\_\_\_\_ IC3:\_\_\_\_\_

VoutMAX:\_\_\_\_\_ VoutMIN:\_\_\_\_\_ MaxPQ1:\_\_\_\_\_

Maximum Short Circuit Current