
Consider the following circuit:

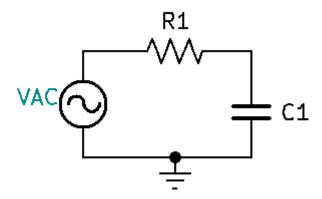

At resonance or Fc, we know that:

• @
$$F_C$$
, $XC_{C1} = R1$

•
$$XC_{C1} = \frac{1}{2\pi FC1}$$

• $R1 = \frac{1}{2\pi F_C C1}$

$$\bullet \quad R1 = \frac{1}{2\pi F_C C1}$$

$$\bullet \quad F_C = \frac{1}{2\pi R1C1}$$

Let's assume that Vgen is equal to 10vp @ 1Khz, and XC_{C1} and R1 both equal to 1K Ω respectively.

•
$$XC_{C1} = 1K\Omega \angle - 90^{\circ}$$

•
$$R1 = 1K\Omega \angle 0^{\circ}$$

•
$$ZT = \sqrt{R1^2 + XC_{C1}^2}$$
, $\angle \tan^{-1} \frac{XC}{R}$
 $\circ ZT = \sqrt{1K^2 + 1K^2}$, $\angle \tan^{-1} \frac{-1K}{1K}$
 $\circ ZT = 1.41421K\Omega$, $\angle -45^\circ$

•
$$IT = \frac{Vgen}{ZT}$$

 $\circ IT = \frac{10vp \angle 0^{\circ}}{1.4142K\Omega \angle -45^{\circ}}$
 $\circ IT = 7.07114mA \angle 45^{\circ}$

•
$$VR = IT \times R$$

$$\circ \quad VR = 7.07114 mA \angle 45^{\circ} \times 1 K\Omega \angle 0^{\circ}$$

$$\circ \quad \textit{VR} = 7.\,07114\textit{vp}\,\angle 45^\circ$$

•
$$VC = IT \times XC_{C1}$$

$$\circ \quad \textit{VC} = 7.07114 \textit{mA} \ \angle 45^{\circ} \ \times 1 \textit{K}\Omega \angle - 90^{\circ}$$

$$\circ \quad \textit{VC} = 7.07114\textit{vp} \, \angle -45^{\circ}$$

With peak voltages and phase angles, we can calculate instantaneous voltages at any point with respect to time.

• $V_{inst} = V max Sin(360Ft \pm \theta)$ $\circ V Gen_{inst} = 10 vp Sin(360 \times 1 Khz \times time \pm 0)$ $\circ V R_{inst} = 7.07 vp Sin(360 \times 1 Khz \times time + 45)$ $\circ V C_{inst} = 7.07 vp Sin(360 \times 1 Khz \times time - 45)$

Time	Vgen = 10vp(sin)(360*1Khz*time+0)	VR = 7.07vp(sin)(360*1khz*time+45)	VC = 7.07vp(sin)(360*1Khz*time-45)
0	0.000	4.999	-4.999
0.00005	3.090	6.299	-3.210
0.0001	5.878	6.983	-1.106
0.00015	8.090	6.983	1.106
0.0002	9.511	6.299	3.210
0.00025	10.000	4.999	4.999
0.0003	9.511	3.210	6.299
0.00035	8.090	1.106	6.983
0.0004	5.878	-1.106	6.983
0.00045	3.090	-3.210	6.299
0.0005	0.000	-4.999	4.999
0.00055	-3.090	-6.299	3.210
0.0006	-5.878	-6.983	1.106
0.00065	-8.090	-6.983	-1.106
0.0007	-9.511	-6.299	-3.210
0.00075	-10.000	-4.999	-4.999
0.0008	-9.511	-3.210	-6.299
0.00085	-8.090	-1.106	-6.983
0.0009	-5.878	1.106	-6.983
0.00095	-3.090	3.210	-6.299
0.001	0.000	4.999	-4.999

