

### **Integrals applied**

1)  $q = \int i \, dt$

2)  $v_c = (1/C) \int i \, dt$

3)  $w = \int p \, dt$

4)  $\Phi = (-1/N) \int v_{ind} \, dt$

5)  $i = (-1/L) \int v_{ind} \, dt$

6)  $i_1 = (-1/M) \int v_2 \, dt$

### **Kirchoff's Laws Applied:**

7) The current Law.

*The sum of the currents toward any point in a circuit at any instant equals zero.*

$$i_g = C \, dv/dt + (v/R) - (1/L) \int v \, dt$$

8) The voltage Law.

*The sum of the voltage drops around a circuit, at any instant, equals zero.*

$$v_g = -L \, di/dt + Ri + (1/C) \int i \, dt$$

261 - Homework: Integrals Applied

- 1) The current in a circuit was  $i = 4t^3$  amps. How many coulombs were transmitted in 3 seconds?
- 2) An  $80\mu\text{f}$  capacitor is charged to 100 volts. We then apply a current  $i_c = 0.04t^3$  amps in the same polarity as the initial charge. After how many seconds will the capacitor voltage reach 225 volts?
- 3) The voltage applied to a circuit was  $v = 2t + 1$  volts. If the current followed the equation  $i = 0.03t$  amperes, find the energy  $w$  delivered from  $t = 0$  to  $t = 50$  seconds.
- 4) A 110 turn winding carries a flux of 0.8 weber. If we now want to vary the flux so that a voltage  $v_{ind} = -5t^2$  volts appears in the winding, what equation must the flux through the winding follow?
- 5) A DC current of 0.3 ampere flows in a 15 henry inductor. Superimposed on this DC is a varying current such that the voltage  $v_{ind} = 120t^{1/3}$  volts appears in the inductor. Find the instantaneous total current when  $t = 1$  second (Assume that the DC and AC currents have the same polarity when  $t = 1$  second).

- 6) An inductance of 8 henrys is connected in series with a  $12\Omega$  resistor. Apply to this circuit a voltage  $v = 20t^2$  volts. If  $i = 0$  when  $t = 0$ , find an equation for  $i$ .
- 7) If we apply a voltage  $v = 90t^{1/2}$  to a circuit consisting of a 30 henry inductance shunted by a 50 ohm resistance, what current flows when  $t = 4$  seconds? (Let  $i = 0$  when  $t = 0$ ).
- 8) If we apply a voltage  $v = 20t^4$  volts across a parallel  $RL$  combination, where  $R = 500\Omega$  and  $L = 40$  henrys, find the total current when  $t = 0.2$  seconds. Let  $i = 4\mu\text{A}$  when  $t = 0$ .
- 9) In a parallel  $RL$  circuit,  $R = 5\Omega$  and  $L = 0.2$  henrys. If a voltage  $v = t^{3/2} + 2$  volts were applied, what would the current  $i$  be when  $t = 4$  seconds? Assume  $i = 0.4$  amps when  $t = 0$ .
- 10) A current  $i = 0.005t^{1/2}$  amps flows in a parallel  $RC$  circuit where  $R = 8.8 \times 10^4 \Omega$  and  $C = 1\mu\text{f}$ . Find a formula for the voltage across the circuit as a function of time  $t$ . Assume the capacitor to be initially discharged.

- 11) The current function  $i = 1 \times 10^{-3} t^{1/2}$  amperes is applied to a series  $RC$  circuit where  $R = 8.8 \times 10^4 \Omega$  and  $C = 1 \mu\text{f}$ . Find a formula for the impressed voltage as a function of time  $t$ . (Assume the initial capacitor charge to be 100 v.)
- 12) A series  $LC$  circuit where  $L = 0.1$  henry and  $C = 100 \mu\text{f}$  has applied to it a current  $i = 0.1\text{A}$  from  $t = 0$  onward. Find (a) the formula for the voltage across the circuit, and (b) the rate of change of the voltage at  $t = 2$  sec. (Assume  $V_c = 0$  when  $t = 0$ ).
- 13) A series circuit has these constants:  $R = 5\text{k}\Omega$ ,  $L = 200$  henrys, and  $C = 20 \mu\text{f}$ . If we supply to the circuit a current  $i = 0.02t^2$  amperes, at what rate does the voltage across the circuit change when  $t = 0.2$  seconds?
- 14) In a series  $RCL$  circuit, let  $R = 10\Omega$ ,  $C = 10,000\mu\text{f}$ , and  $L = 10$  henrys. Through this circuit we pass a current  $i = 1 - t^{1/2}$  amps. Find the total voltage  $v$  across this circuit when  $t = 4$  seconds. Assume  $v = 0.25$  volts when  $t = 1$  second.