

1. The current in a circuit was $i = 4t^3$ amps. How many Coulombs were transmitted in 3 seconds?

$$q = \int i \, dt$$

$$q = \int 4t^3$$

$$q = \frac{4t^4}{4} + C$$

$$q = t^4 + C$$

$$q = (3)^4 + 0$$

$$\boxed{q = 81 \text{ coulombs}} \quad \star$$

2. An 80- μ F capacitor is charged to 100 volts. We then apply a current $i = 0.04t^3$ amps in the same polarity as the initial charge. After how many seconds will the capacitor voltage reach 225 volts?

$$V_C = \frac{1}{C} \int i \, dt$$

$$225 = \frac{1}{80 \mu\text{F}} \int 0.04t^3 \, dt$$

$$225 = \frac{1}{80 \mu\text{F}} \left(\frac{0.04t^4}{4} \right) + \frac{C}{+ 100 \text{ V}}$$

$$225 = \frac{0.04t^4}{320 \times 10^{-6}} + 100$$

$$225 - 100 = 125t^4$$

$$125 = 125t^4$$

$$(t^4 = 1)^{\frac{1}{4}}$$

$$\boxed{t = 1 \text{ sec}} \quad \star$$

3. The voltage applied to a circuit was $v = 2t + 1$ volts. If the current followed the equation $i = 0.03t$ amperes, find the energy w delivered from $t = 0$ to $t = 50$ seconds.

$$w = \int p \, dt$$

$$w = \int (2t + 1)(.03t) \, dt$$

$$w = \int .06t^2 + .03t \, dt$$

$$w = \frac{.06t^3}{3} + \frac{.03t^2}{2} + C$$

$$w = \frac{.06(50)^3}{3} + \frac{.03(50)^2}{2} + 0$$

$$w = 2.5 \times 10^3 + 37.5 + 0$$

$$w = 2537.5 \text{ K} \overset{\text{WATTS}}{\underset{\text{joules}}{\text{J}}} \quad \star$$

4. A 110 turn winding carries a flux of 0.8 webers. If we now want to vary the flux so that a voltage $v_{ind} = -5t^2$ volts appears in the winding, what equation must the flux through the winding follow?

$$\phi = \frac{-1}{N} \int v_{ind} \, dt$$

$$\phi = \frac{-1}{110} \int -5t^2 \, dt$$

$$\phi = \frac{-1}{110} \left(\frac{-5t^3}{3} \right) + 0.8$$

$$\phi = \frac{5t^3}{330} + .8$$

$$\phi = 15.152 \times 10^{-3} t^3 + .8$$

OR

$$\phi = \frac{t^3}{66} + .8 \quad \star$$

- 5.) a DC current of 0.3 ampere flows in a 15 henry inductor. Superimposed on this DC is a varying current such that the voltage $v_{ind} = 120t^{4/3}$ volts applied in the inductor. Find the instantaneous total current when $t = 1$ second. (assume that the DC and AC currents have the same polarity when $t = 1$ second).

$$i = \frac{-1}{L} \int v_{ind} \quad t = 1 \text{ second}$$

$$i = \frac{-1}{15} \int 120t^{4/3}$$

$$i = \frac{-1}{15} \left(\frac{120t^{4/3}}{\frac{4}{3}} \right) + .3$$

$$i = \frac{+3(120)(t)^{4/3}}{15(4)} + .3 \quad \text{same polarity}$$

$$i = 6 + .3$$

$$\boxed{i = 6.3 \text{ amps}} \quad \star$$

- 6.) An inductance of 8 henrys is connected in series with a 12 ohm resistor. Apply to this circuit a voltage $V = 20t^2$ volts. If $i = 0$ when $t = 0$, find an equation for i .

$$iR = C \frac{dv}{dt} + \frac{V}{R} + \frac{1}{L} \int V dt$$

$$iR = \frac{V}{R} + \frac{1}{L} \int V dt$$

$$iR = \frac{20t^2}{12} + \frac{1}{8} \left(\frac{20t^3}{3} \right) + 0 \quad + C$$

$$iR = \frac{5t^2}{3} + \frac{20t^3}{24} + 0$$

$$\boxed{iR = \frac{5t^2}{3} + \frac{5t^3}{6}} \quad \star$$

7. If we apply a voltage $v = 90t^{1/2}$ to a circuit consisting of a 30 henry inductor shunted by a 50 ohm resistance. What current flows when $t = 4$ seconds? (Let $i = 0$ when $t = 0$)

$$i_g = \frac{V}{R} + \frac{1}{L} \int v dt$$

$$i_g = \frac{90t^{1/2}}{50} + \frac{1}{30} \int 90t^{1/2}$$

$$i_g = \frac{90(4)^{1/2}}{50} + \frac{1}{30} \left(\frac{90t^{3/2}}{\frac{3}{2}} \right) + C$$

$$i_g = \frac{9(4)^{1/2}}{5} + \frac{2(90)(4)^{3/2}}{30(3)} + 0$$

$$i_g = 3.6 + 16 + 0$$

$$\boxed{i_g = 19.6 \text{ amps}} \star$$

8. If we apply a voltage $v = 20t^4$ volts across a parallel R & L combination, where $R = 500 \Omega$ and $L = 40$ henrys, find the total current when $t = 0.2$ seconds. Let $i = 4 \mu A$ when $t = 0$.

$$i_g = \frac{V}{R} + \frac{1}{L} \int v dt$$

$$i_g = \frac{20t^4}{500} + \frac{1}{40} \left(\frac{20t^5}{5} \right) + C$$

$$i_g = \frac{20(.2)^4}{500} + \frac{1}{40} \left(\frac{20(.2)^5}{5} \right) + 4 \mu A$$

$$i_g = 64 \mu A + 32 \mu A + 4 \mu A$$

$$\boxed{i_g = 100 \mu A} \star$$

9. In a parallel RL circuit, $R = 5 \Omega$ and $L = 0.2$ henrys. If a voltage $v = t^{3/2} + 2$ volts were applied, what would the current i be when $t = 4$ seconds? Assume $i = 0.4$ amps when $t = 0$.

$$i_g = \frac{1}{R} + \frac{1}{L} \int v dt$$

$$i_g = \frac{t^{3/2} + 2}{5} + \frac{1}{0.2} \int t^{3/2} + 2 dt$$

$$i_g = \frac{4^{3/2} + 2}{5} + \frac{1}{0.2} \left(\frac{t^{5/2}}{5/2} + 2t \right) + 0.4$$

$$i_g = 2 + \frac{1}{0.2} \left(\frac{2(4^{5/2})}{5} + 2(4) \right) + 0.4$$

$$i_g = 2 + \frac{1}{0.2} (12.8 + 8) + 0.4$$

$$i_g = 2 + 104 + 0.4$$

$$i_g = 106.4 \text{ amps} \quad \star$$

10. A current $i = 0.005 t^{1/2}$ amps flows in a parallel RC circuit where $R = 8.8 \times 10^4 \Omega$ and $C = 1 \mu\text{F}$. Find a formula for the voltage across the circuit as a function of time t . Assume the capacitor to be initially discharged.

$$v_g = Ri + \frac{1}{C} \int i dt$$

$$v_g = (8.8 \times 10^4)(0.005 t^{1/2}) + \frac{1}{1 \mu\text{F}} \left(\frac{0.005 t^{3/2}}{3/2} \right) + 0$$

$$v_g = 440 t^{1/2} + \frac{10 \times 10^{-3} t^{3/2}}{3 \times 10^{-6}}$$

$$v_g = 440 t^{1/2} + 3.333 \times 10^3 t^{3/2} \quad \star$$

11. The current function $i = 1 \times 10^{-3} t^{1/2}$ amperes is applied to a series RC circuit where $R = 8.8 \times 10^4 \Omega$ and $C = 1 \mu F$. Find a formula for the impressed voltage as a function of time t . (Assume the initial capacitor charge to be 100v.)

$$V_g = Ri + \frac{1}{C} \int i dt = (8.8 \times 10^4)(1 \times 10^{-3} t^{1/2}) + \frac{1}{1 \mu F} \left(\frac{1 \times 10^{-3} t^{3/2}}{\frac{3}{2}} \right) + 100$$

$$V_g = 88 t^{1/2} + 666.667 t^{3/2} + 100$$

$$V_g = 88 t^{1/2} + \frac{2 \times 10^{-3} t^{3/2}}{3 \times 10^{-6}} + 100$$

★

12. A series LC circuit where $L = 0.1$ henry and $C = 100 \mu F$ has applied to it a current $i = 0.1 a$ from $t = 0$ onward. Find (a) the formula for the voltage across the circuit, and (b) the rate of change of the voltage at $t = 2$ sec. (Assume $V_c = 0$ when $t = 0$)

$$V_g = L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt \quad i = 0.1 a t^0$$

$$V_g = 0 + 0 + \frac{1}{100 \mu F} \left(\frac{0.1 t^1}{1} \right) \quad \frac{di}{dt} = 0$$

$$V_g = \frac{0.1 t}{100 \times 10^{-6}}$$

a) $V_g = 1000 t$ ★

$$\text{Rate of Change} = \frac{dV}{dt} \quad V_g = 1000 t$$

$$\frac{dV}{dt} = 1000 t^{1-1} = 1000 t^0 = 1000$$

$$\frac{dV}{dt} = 1000 V \quad ★$$

13. A series circuit has three constants: $R = 5K\Omega$, $L = 200$ Henry, and $C = 20\mu F$. If we supply to the circuit a current $i = 0.02t^2$ amperes, at what rate does the voltage across the circuit change when $t = 0.2$ seconds?

$$V_g = L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt \quad i = 0.02t^2$$

$$V_g = 200(.04t) + 5K(.02t^2) + \frac{1}{20\mu F} \left(\frac{.02t^3}{3} \right) \frac{di}{dt} = .04t$$

$$V_g = 8t + 100t^2 + 333.33t^3$$

$$\frac{dV}{dt} = 8 + 200t + 999.999t^2$$

$$\frac{dV}{dt} = 8 + 200(.2) + 1K(.2)^2$$

40 + 40

$$\boxed{\frac{dV}{dt} = 88V/s} \quad \star$$

14. In a series AC circuit, let $R = 10\Omega$, $C = 10,000\mu F$, and $L = 10$ henrys. Through this circuit we pass a current $i = 1 - t^{1/2}$ amps. Find the total voltage V across this circuit when $t = 4$ seconds. Assume $V = 0.25$ volts when $t = 1$ second.

$$V_g = L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt \quad i = 1 - t^{1/2}$$

$$.25V = 10\left(-\frac{1}{2}t^{-1/2}\right) + 10\left(1 - t^{1/2}\right) + 100\left(t - \frac{2t^{3/2}}{3}\right) \frac{di}{dt} = \frac{-1}{2}t^{-1/2}$$

$$.25V = -5 + 33.333 + C \quad \int 1 - t^{1/2} = \frac{t}{1} - \frac{t^{3/2}}{3/2}$$

$$C = -28.083V$$

$$V_g = L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt$$

$$V_g = 10\left(-\frac{1}{2}t^{-1/2}\right) + 10\left(1 - t^{1/2}\right) + 100\left(t - \frac{2t^{3/2}}{3}\right) \div 28.083$$

$$-V_g = -2.5 + 10 + 133.333 - 46.333 - 28.083$$

$$\boxed{V_g = -173.9V} \quad \star$$

Ch 14

$$q = \int i dt \text{ coulombs}$$

$$v = \frac{1}{C} \int i dt \text{ volts}$$

$$w = \int p dt \text{ joules}$$

$$\phi = -\frac{1}{N} \int v_{ind} dt \text{ webers}$$

$$i_L = -\frac{1}{L} \int v_{ind} dt \text{ amperes}$$

$$i_1 = -\frac{1}{m} \int v_2 dt \text{ amperes}$$

Problems 14-1

1. The current in a circuit was $i = 4t^3$ amperes. How many coulombs were transmitted in 3 seconds?

$$q = \int i dt = \int 4t^3 dt$$

$$q = \frac{4t^4}{4} = \frac{4(3)^4}{4} = 3^4 = 81$$

$$q = 81 \text{ coulombs (K)}$$

3. An $80 \mu\text{F}$ capacitor is charged to 100V . We then supply to the capacitor a current $i = 0.04t^3$ amperes, in the same polarity as the initial charge. After what time interval in seconds does the capacitor voltage reach 225 volts?

$$v_C = \frac{1}{C} \int i dt = 225\text{V} = \frac{1}{80 \mu\text{F}} \int 0.04t^3 dt$$

$$\frac{225\text{V}}{1} \cdot \frac{80 \mu\text{F}}{1} = \int 0.04t^3 dt$$

$$18 \times 10^3 = \int 0.04t^3$$

$$18 \times 10^3 = \frac{0.04t^4}{4} + 100\text{V}$$

$$18 \times 10^3 - 100 = \frac{0.04t^4}{4}$$

$$-99.982 = \frac{0.04t^4}{4}$$

$$-399.928 = 0.04t^4$$

$$-9.9982 \times 10^3 = t^4 \rightarrow$$

$$t = 1.5 \times 10^3$$

Problems 14-1

#3 Continued.

$$C = 80 \mu\text{F} \quad \text{initial Charge} = 100 \text{ V} \quad i = 0.04t^3 \quad (K)$$

$$V_C = 225 \text{ V} \quad t = ?$$

$$V_C = \frac{1}{C} \int i \, dt$$

$$225 \text{ V} = \frac{1}{80 \mu\text{F}} \int .04t^3 \, dt$$

$$225 \text{ V} = \frac{1}{80 \mu\text{F}} \left(\frac{.04t^4}{4} \right) + 100 \text{ V}$$

$$125 \text{ V} = \frac{1}{80 \mu\text{F}} \times \frac{.04t^4}{4}$$

$$125 \text{ V} = \frac{.04t^4}{80 \mu\text{F} \times 4}$$

$$125 \text{ V} = \frac{.04t^4}{320 \times 10^{-6}}$$

$$125 = 125t^4$$

$$t^4 = \frac{125}{125}$$

$$(t^4 = 1)^{\frac{1}{4}}$$

$$t = 1^{\frac{1}{4}}$$

$$\boxed{t = 1}$$

#5. The voltage applied to a circuit was $V = 2t + 1$ volts & the current followed the equation $i = 0.03t$ amperes, find the energy w delivered from $t = 0$ to $t = 50$ seconds.

$$V = 2t + 1 \quad i = 0.03t \quad \text{Find } w \quad t = 0 \quad t = 50 \text{ seconds}$$

$$w = \int p \, dt \quad P = I \cdot V \quad (.03t)(2t + 1)$$

$$w = \int .06t^2 + .03t$$

$$w = \frac{.06t^3}{3} + \frac{.03t^2}{2}$$

$$w = 2.5K + 37.5$$

$$\boxed{w = 2,537.5 \text{ joules}}$$

Problems 14-1

- #7. A 110 turn winding carries a flux of $(0.8)^K$ webers. If we now want to vary the flux so that a voltage $v_{ind} = -5t^2$ volts appears in the winding, what equation must the flux through the winding follow?

$$N = 110 \quad K = .8 \text{ webers} \quad v_{ind} = -5t^2$$

$$\Phi = -\frac{1}{N} \int v_{ind} dt$$

$$\Phi = -\frac{1}{110} \int -5t^2$$

$$\Phi = \frac{-1}{110} \int -5t^2$$

$$\Phi = -\frac{1}{110} \left(\frac{-5t^3}{3} \right) + .8$$

$$\Phi = \frac{+5t^3}{330} + .8$$

$$\boxed{\Phi = \frac{t^3}{66} + .8}$$

- #9. A direct current of 0.3 ampere flows in a 15 henry inductor. Superimposed on this direct current is a varying current such that a voltage $v_{ind} = 120t^{1/3}$ volts appears in the inductor. Find the instantaneous total current when $t = 1$ second. (assume that the steady and the varying currents have the same polarity when $t = 1$ second.)

$$.3 \text{ amp flows} = K \quad L = 15 \text{ henry} \quad v_{ind} = 120t^{1/3} \text{ volts} \quad t = 1 \text{ second}$$

Find total current.

$$i_L = -\frac{1}{L} \int v_{ind} dt$$

$$i_L = -\frac{1}{15} \int 120t^{1/3} dt$$

$$i_L = -\frac{1}{15} \left(\frac{120t^{4/3}}{(4/3)} \right) + K$$

$$i_L = -\frac{1}{15} \left(\frac{3 \cdot 120t^{4/3}}{4} \right) \overset{\text{Same polarity}}{\downarrow} (+) .3$$

$$i_L = +6 + .3$$

$$\boxed{i_t = 6.3 \text{ amps or } -6.3 \text{ amps}}$$