

ROBOTICS AND COMMUNICATIONS SYSTEMS ENGINEERING TECHNOLOGY  
PUSH-PULL AMPLIFIERS LAB  
3RD SEMESTER, SR. INSTRUCTOR TIM LEISHMAN

**General Objective:**

Upon completion of this lab, the student will be able to:

- A. Calculate voltages, currents, gains, and impedances of Push-Pull amplifier circuits.
- B. Construct, measure, and demonstrate the proper use of the test equipment.

**References:**

- Theory notes
- First Year Text & Lab books

**Check-Off Sheet:**

- [Check-Off Sheet](#)

**Specific Objectives:**

1. Push-Pull Amplifier
  - a. Design a Push-Pull circuit to accept  $V_{in}$  from the variable gain Diff-Amp form your previous lab and to drive audio speaker for  $R_L$ .
  - b. Show all calculations and schematic.
  - c. **Instructor Check**
  - d. Using equivalent load resistor, measure gain and frequency response of the amplifier.
  - e. **Instructor Check**
  - f. Functionally test the circuit using a Speaker
  - g. **Instructor Check**
2. Complete Conclusion and submit completed Check-Off sheet and Lab writeup in Moodle.

