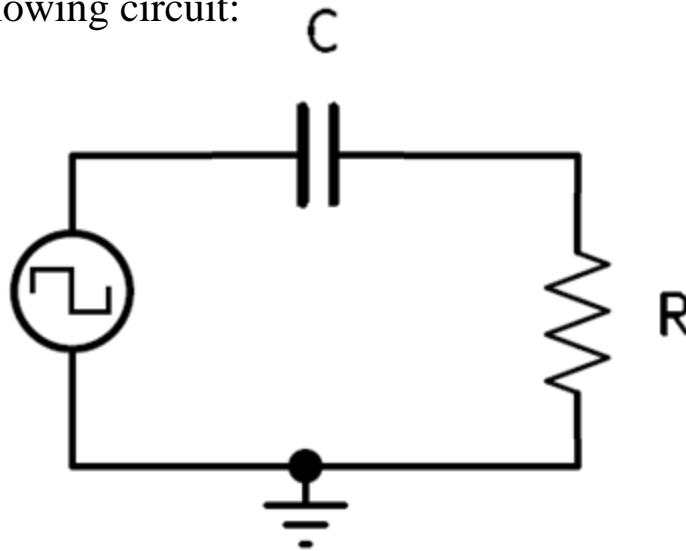


Consider the following circuit:



Differentiation

- “Differentiation is a measure of rate of change.” (Bell p.56)
- There is more than enough time for the capacitor to fully charge and discharge.
 1. PW or PS is greater than 5τ .
 2. “When RC is less than one-tenth of the pulse width, the capacitor is charged very rapidly. Only a brief pulse of current is necessary to charge and discharge the capacitor at the beginning and end of the pulse. The resultant waveform of the resistor voltage is a series of positive and negative spikes at the pulse leading and lagging edges, respectively.” (Bell p.56)
 3. The standard formulas for designing an Integrating RC circuit is:
 - $RC = \tau$
 - 50% DC, $PW = PS$
 - $PW = \text{Time to charge}, PS = \text{Time to discharge}$
 - $RC = (\frac{1}{10} PW)$ (Differentiation in terms of τ)
 - $\text{Time} = 10 \times \tau$ (Differentiation formula in terms of Time, lots of Time to charge or discharge)

See Image:

- Is **not** a Differentiator, the capacitor is not fully charging or discharging.
- Is **not** an Differentiator, $\tau = PW$. 63% charge and discharge
- Is a **Differentiator**, the capacitor is fully charging and discharging within a relatively fast amount of time when comparted to the PW and PS and the resulting resistor voltage appears as positive and negative going spikes.

Differentiating Circuits

