

ROBOTICS AND COMMUNICATIONS SYSTEMS ENGINEERING TECHNOLOGY
PUSH-PULL AMPLIFIERS LAB
3RD SEMESTER, SR. INSTRUCTOR TIM LEISHMAN

General Objective:

Upon completion of this lab, the student will be able to:

- A. Calculate voltages, currents, gains, and impedances of Push-Pull amplifier circuits.
- B. Construct, measure, and demonstrate the proper use of the test equipment.

References:

- Theory notes
- First Year Text & Lab books

Check-Off Sheet:

- [Check-Off Sheet](#)

Specific Objectives:

1. Push-Pull Amplifier
 - a. Design a Push-Pull circuit to accept V_{in} from the variable gain Diff-Amp from your previous lab. Your Push-Pull will be designed to drive a 5-watt, 8-ohm speaker.
 - b. Show all calculations.
 - c. **Instructor Check**
 - d. Using an equivalent load resistor, measure gain and frequency response of the amplifier.
 - e. **Instructor Check**
 - f. Functionally test the circuit using an instructor issued speaker
 - g. **Instructor Check**
2. Complete Conclusion and submit completed Check-Off sheet and Lab writeup in Moodle.

