
**High Frequency Distortion** is caused by **parallel capacitance** and results in an increase in the **Rise & Fall Times** of a square wave.


• Consider the following circuit

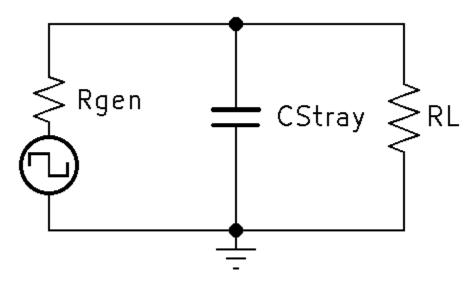

• Using Square-Wave analysis and a known rise time, we can calculate the circuits high critical frequency by dividing .35/(rise time).

$$\circ f_{CH} = \frac{0.35}{tr}$$

$$\circ tr = \frac{0.35}{f_{CH}}$$

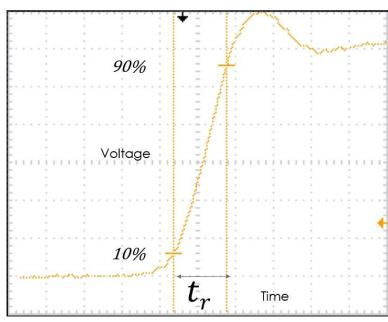

## **Deriving the High Critical Frequency Formula:**

**Givens:** 

- ☐ Rise Time is measured from 10% to 90%
- $\square$  Rise Time = tr
- $\Box$  Frequency Cutoff High = fch
- $\Box$   $fch = \frac{0.35}{tr}$

**Known Formulas from Second Semester:** 

• 
$$X_c = \frac{1}{2\pi FC}$$

• 
$$Vc = vfin - (vfin - vin)e^{\frac{-t}{RC}}$$

Knowing that at Critical Frequency Xc is equal to R, we can derive the following

• 
$$Xc = \frac{1}{2\pi FC}$$

• @ 
$$F_{CH}$$
,  $R = XC$ 

• 
$$R = \frac{1}{2\pi FC}$$

• 
$$F_{CH} = \frac{1}{2\pi RC}$$

Rise time is the time measured from 10% to 90% of the waveform amplitude. Therefore, If you set the equation in terms of rise time we get the following

• 
$$Vc = vfin - (vfin - vin)e^{\frac{-t}{RC}}$$

• 
$$Vc = .9vfin$$

• 
$$vin = .1 \ vfin$$

• 
$$t = tr$$

And Therefore,

• 
$$.9vfin = vfin - (vfin - .1 vfin)e^{\frac{-tr}{RC}}$$

- $.9vfin = vfin (vfin .1 vfin)e^{\frac{-tr}{RC}}$
- $.9vfin vfin = (-vfin + .1 \ vfin)e^{\frac{-tr}{RC}}$
- $-.1vfin = (-.9 \ vfin)e^{\frac{-tr}{RC}}$
- $\bullet \quad \frac{-.1vfin}{-.9vfin} = e^{\frac{-tr}{RC}}$
- $\frac{1}{9} = e^{\frac{-tr}{RC}}$
- $\ln \frac{1}{9} = \frac{-tr}{RC}$
- $-2.19722 = \frac{-tr}{RC}$
- $RC = \frac{tr}{2.19722}$

We have solved for two formulas, now we can solve the final equation.

- $RC = \frac{tr}{2.19722}$  &  $F_{CH} = \frac{1}{2\pi RC}$
- $F_{CH} = \frac{1}{2\pi \frac{tr}{2.19772}}$
- $F_{CH} = \frac{2.19772}{2\pi tr}$
- $F_{CH} = \frac{.349778}{tr}$  OR  $F_{CH} = \frac{.35}{tr}$

## **References**:

Bell, D. A. (1997). Solid state pulse circuits. Sarnia, ON: David A. Bell.