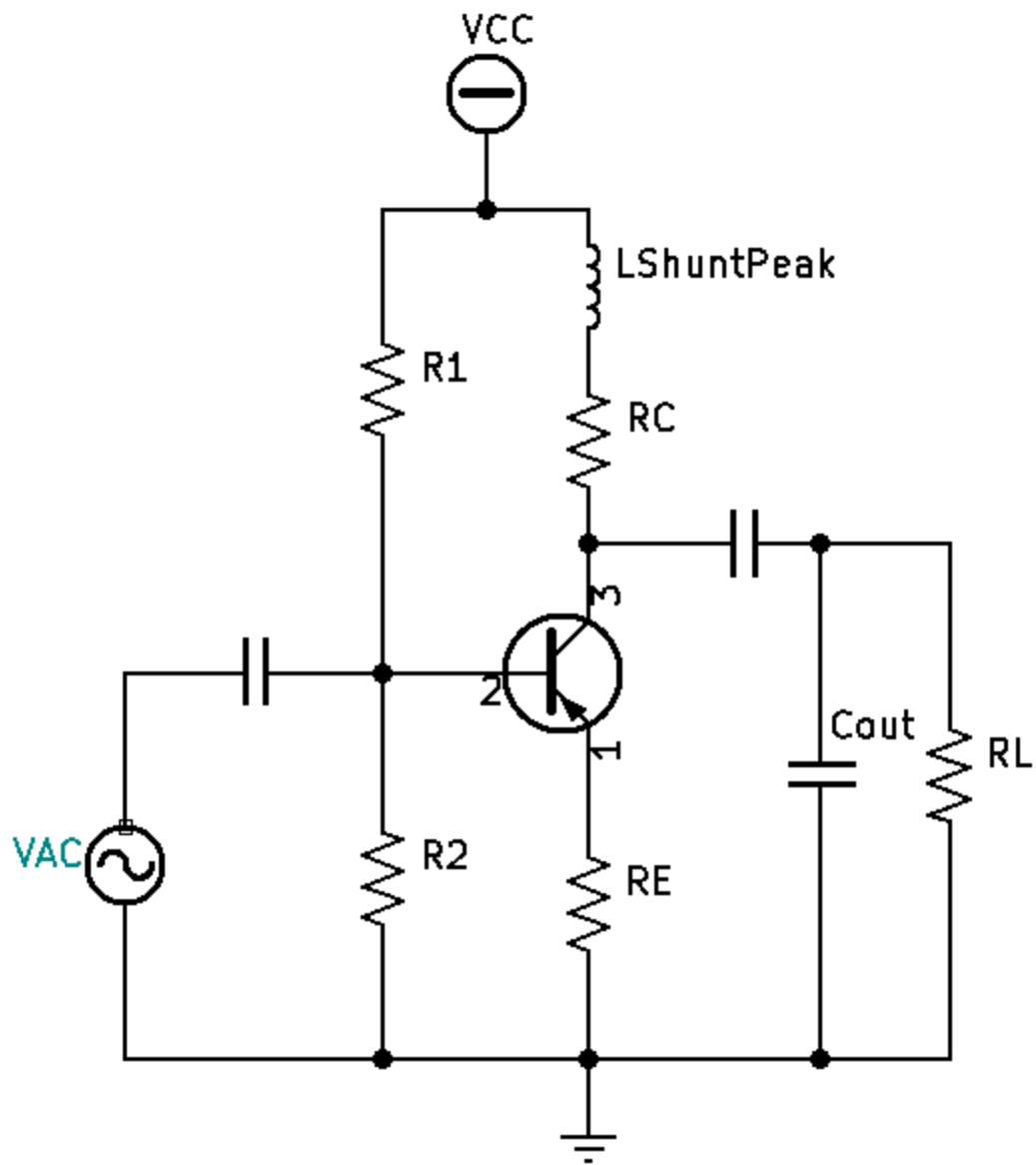


Shunt Peaking:



- Calculate and or Measure your existing f_{ch} .
- Determine your actual C_{out} based off measured f_{ch} .
- Design Shunt Peaking of optimal flatness using an Improvement Factor of $k = 1.414$

○ Calculate $newf_{ch}$:

$$\blacksquare newf_{ch} = oldf_{ch} \times k$$

$$\blacksquare newf_{ch} = oldf_{ch} \times 1.414 \text{ (optimal flatness)}$$

○ Calculate L:

$$\blacksquare \text{ Make } fr = .707(oldf_{ch})$$

$$\blacksquare fr = \frac{1}{2\pi\sqrt{LC}}$$

$$\blacksquare .707(oldf_{ch}) = \frac{1}{2\pi\sqrt{LC_{out}}}$$

$$\blacksquare \sqrt{LC_{out}} = \frac{1}{2\pi(.707oldf_{ch})}$$

$$\blacksquare LC_{out} = \left(\frac{1}{2\pi(.707oldf_{ch})}\right)^2$$

$$\blacksquare L = \frac{\left(\frac{1}{2\pi(.707oldf_{ch})}\right)^2}{C_{out}}$$

$$\blacksquare L = C_{out}^{-1} \left(\frac{1}{2\pi(.707oldf_{ch})}\right)^2$$