

15. A series circuit consists of a 22 H inductor and a 68  $\Omega$  resistor. A current  $i = 2t^2 + t$  exists in this combination. After what time  $t$  does the voltage across the combination equal 375 volts?  $t = 1.784s$

16. A voltage  $v = t^3 + 1,000$  volts appears across a parallel RC combination, where  $R = 2 \text{ M}\Omega$  and  $C = 1 \mu\text{f}$ . Find the resulting current  $i_g$  at any time  $t$ .  
 $i_g = 3 \times 10^{-6}t^2 + 500 \times 10^{-9}t^3 + 500 \times 10^{-6}$

17. A transistor operates into a load resistance of 2.2 k $\Omega$ . The shunt capacitance in the circuit equals 70 pF, as measured at the collector. Over a certain interval the output voltage supplied by the transistor equals  $v = 1 \times 10^7 t + 30$  volts. Find the collector signal current when  $t = 10 \mu\text{s}$ .  
 $i_c = 59.791 \text{ mA}$

18. A current  $i = 10t^{1/2} + 0.1$  amps flows through a series RL circuit, where  $R = 800 \Omega$  and  $L = 320 \text{ H}$ . Find the voltage  $v_g$  across this circuit when  $t = 0.04$  second.  $v_g = -6.32 \text{ Kv}$

19. A transistor collector has a load resistor of 4.7 k $\Omega$  with a compensation inductor  $L = 20 \text{ mH}$  in series with the resistor. The current  $i$  through the combination equals  $2.5 \times 10^4 t + 0.01$  amps. Find the voltage across the RL circuit when  $t = 25 \text{ ns}$ .  $v_g = -450.063 \text{ v}$

20. A 27 k $\Omega$  resistor shunts a 33  $\mu\text{f}$  capacitor. The applied voltage  $v$  equals  $300t^2$  volts. At what time  $t$  does the total current  $i$  equal 84 mA?  $t = 1.999s$

21. The voltage applied across a capacitor of 0.2  $\mu\text{f}$  was  $v = 5 - 3t^2$  volts. The energy stored in a capacitor is  $w = Cv^2/2$  joules. Find a formula for  $dw/dt$  in this capacitor.  $\frac{dw}{dt} = -1.2 \times 10^{-6}t(5 - 3t^2)$  OR  $= 3.6 \times 10^{-6}t^3 - 6 \times 10^{-6}t$

22. The intensity  $I$  of light from a tungsten filament varies with the applied voltage according to  $I = Av^{3.7}$ , where  $A$  is a constant and  $v$  is the applied voltage. If  $v = t - 2t^2$ , find a formula for  $dI/dt$ .

$$\frac{di}{dt} = 3.7a(t - 2t^2)^{2.7}(1 - 4t)$$

23. When a length  $l$  meters of a conductor moves at a speed of  $v$  meters per second in a magnetic field of uniform flux density  $\beta$  teslas, a voltage is induced equal to  $v = -\beta lv$  volts. If  $v = 10$  meters per second,  $l = 0.3$  meter, and  $\beta$  varies over a certain interval according to  $\beta = 1/t^2$ , find  $dv/dt$  when  $t = 0.5$  seconds.  $\frac{dv}{dt} = 48v/s$

24. The frequency of a certain crystal oscillator varies with temperature  $T$  according to  $f = f_a[1 + k(T - T_a)]$ , where  $f_a$  is the frequency at an initial temperature  $T_a$  and  $k$  is a constant of the crystal. If  $T$  varies with time ( $t$  minutes) according to  $T = 55 + 0.01t^2$ , how fast does  $f$  change when  $t = 10$ ?  $\frac{df}{dt} = fak(.2)$

25. The wavelength  $\lambda$  meters of a radio wave traveling at a speed  $c = 3 \times 10^8$  meters per second varies with the frequency according to  $\lambda = c/f$ . If  $f = 1 \times 10^8 + (5 \times 10^7)t^{1/2}$  hertz find a formula for  $d\lambda/dt$ .

$$\frac{d\lambda}{dt} = \frac{-7.5 \times 10^{15}}{(1 \times 10^8 + 5 \times 10^7 t^{1/2})^2 t^{1/2}}$$

26. The voltage  $v$  across a varying resistor  $r$ , carrying a fixed current  $I$ , is  $v = Ir$ . If  $r$  varies with time  $t$  according to  $r = t^3 + 5$ , find a formula for  $dv/dt$  in this capacitor.  $\frac{dv}{dt} = 3t^2 I$

27. The mutual inductance between two windings is  $M = N_2 \phi_2 / i_1$ , where  $i_1$  is the current in one of the windings and  $N_2$  and  $\phi_2$  are the number of turns of the second winding and the flux linking it to the first winding. If  $i_1$  and  $N_2$  are constant, and if the second winding moves so that  $\phi_2$  varies with time  $t$  seconds according to  $\phi_2 = t^3 - 2t$ , find a formula for  $dM/dt$ .

$$\frac{dm}{dt} = \frac{n_2}{i_1} (3t^2 - 2)$$

28. A copper wire of diameter  $d$  and length  $s$  has a resistance of  $r = ks/d^2$ , where  $k$  is a constant. Suppose a sliding wire changes the length so that  $s = t^2 - 0.6t$ , where  $t$  is in seconds. Find a formula for  $dr/dt$ .

$$\frac{dr}{dt} = \frac{k}{d^2} (2t - 0.6)$$

29. The force between two charged particles having fixed charges  $Q_1$  and  $Q_2$  varies with the distance separating them according to  $F = Q_1Q_2/4\pi\epsilon s^2$ . If  $\epsilon$  is a constant, and if  $s$  varies with time as  $s = 6t^{3/2}$ , find a formula for  $dF/dt$ .

$$\frac{dF}{dt} = \frac{-Q_1Q_2}{48\pi\epsilon t^{5/2}}$$