
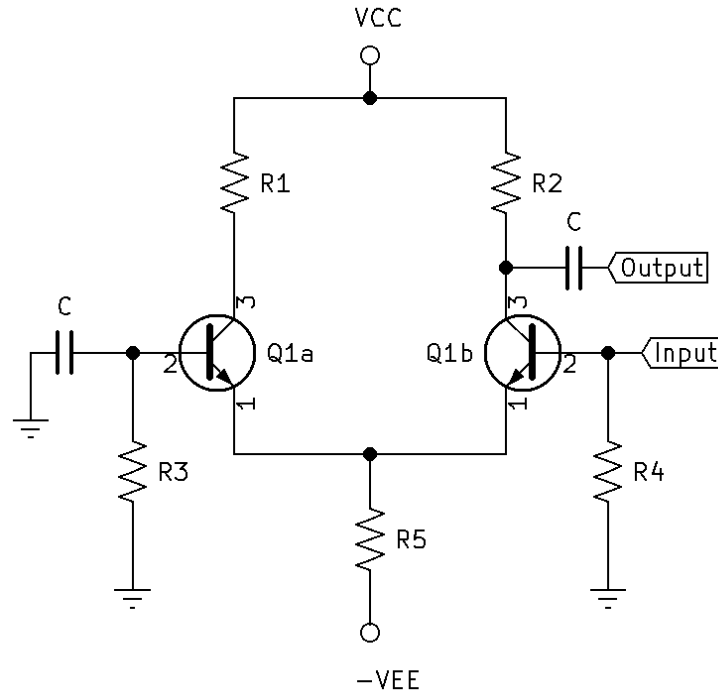


- A Differential Amplifier is an amplifier that produces outputs that are a function of the difference between two inputs.
- Transistors are Beta matched.
- RCs are equal, ($R1=R2$)
- RBs are equal, ($R3=R4$)
- R_{E5} is equal to $2 \times I_E$.

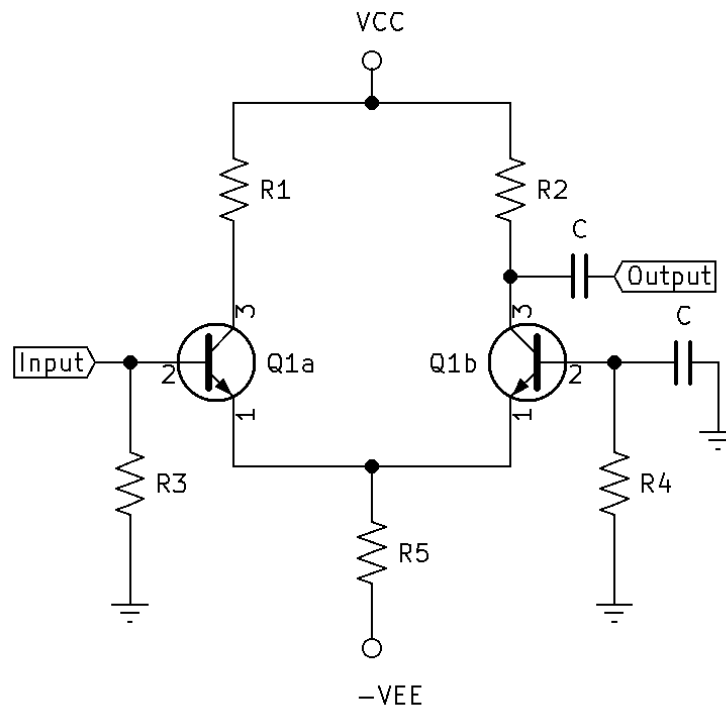
- Single-Ended Differential Input: The Diff-Amp is operated with one input grounded and signal voltage is applied to the other input.
 - Below is an example of Single-Ended Differential Input Inverting Amplifier.




- Below is an example of Single-Ended Differential Input Non-Inverting Amplifier.



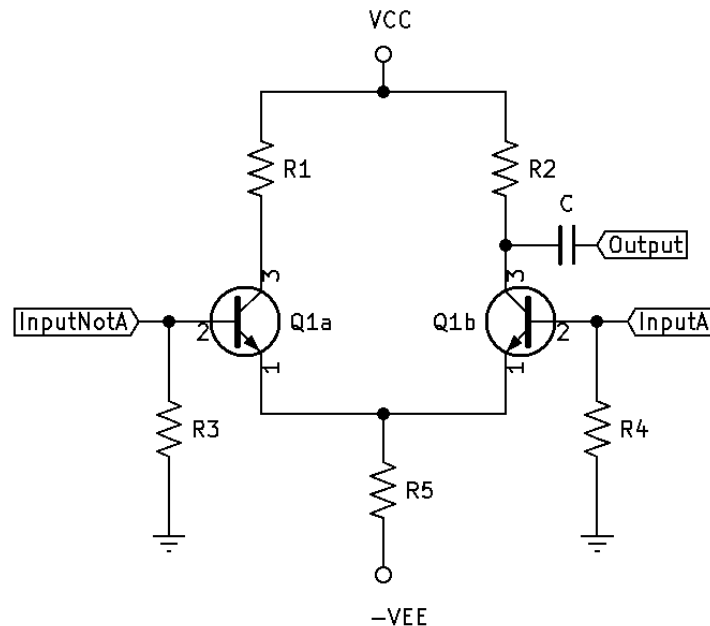- Double-Ended Differential Inputs: Two 180° out of phase signals with the same amplitude and frequency are applied to the inputs. The gain resultant is $2 \times \Delta v$.



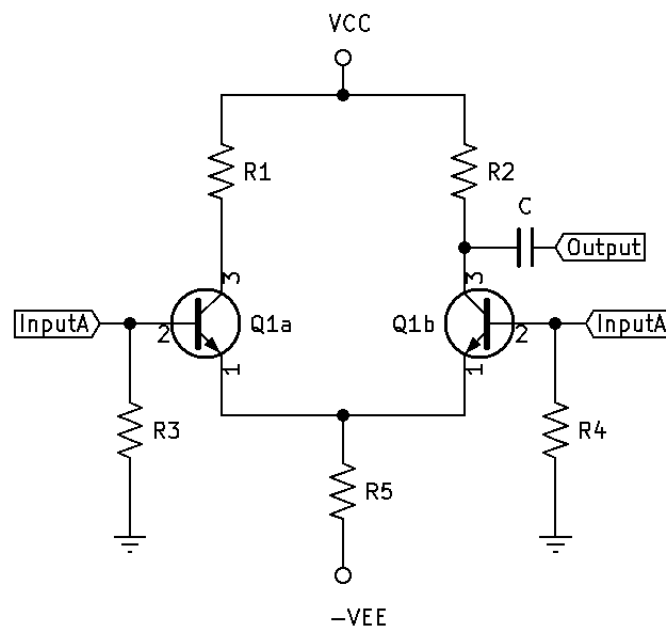- Common-Mode: Two in-phase signals with the same amplitude and frequency are applied to the inputs. The gain resultant is $\Delta v \approx 0$.



- CMRR (Common-Mode Rejection Ration): The measure of an amplifiers ability to reject Common-Mode signals.
- $CMRR_{dB} = 20 \log \left(\frac{\Delta v_{cm}}{\Delta v_{diff}} \right)$

